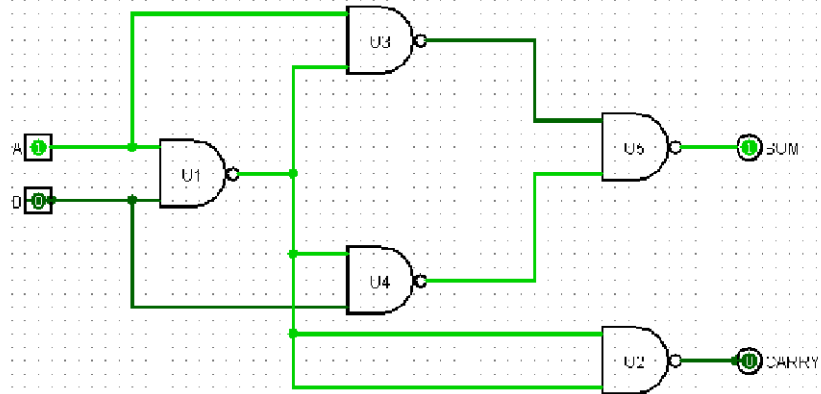


Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	0	1
1	0	1	0
1	1	0	1



FULL ADDER USING NAND GATES